

Exam 1



_____,
Last Name

_____,
First Name

Instructions:

- Turn off **cell phones**, **beepers** and other noise making devices.
- Show **all** work on the **front** of the test papers. If you need more room, make a clearly indicated note on the front of the page, "MORE ON BACK", and use the back. The back of the page will **not** be graded without an indication on the front.
- You may use any of your XMEGA documents with **limited** added material; highlighting and tagging is permissible. You may **not** use any notes (mine or yours), examples, homework, labs, books, calculators, computer, electronic devices, etc.
- **CLEARLY** write your name at the top of **this** test page (and, if you remove the staple, all others). Be sure your exam consists of **11** distinct pages. Sign your name and add the date below. (If we struggle to read your name, you will lose points.)
- The space provided does **not** necessarily represent the amount of writing needed.
- You must pledge and sign this page in order for a grade to be assigned.
- In programs, the use of comments results in **more** partial credit.
- **Read** each question **carefully** and **follow the instructions**.
- The point values for problems may be changed at prof's discretion.
- Part of your grade on tests, quizzes, labs, etc. is based not only on solving the problem you are presented with, but the manner in which you solve it. For example, there is a difference between two programs that meet the given specifications, where one is an elegant, extensible 20-line solution, while the other is an obfuscated 100-line program (that also meets the specifications, but would be difficult to extend later). Just as your future employer would value the latter program less than the first, so will I in grading your assignments.
- This exam counts for **20.7-24.3%** of your total grade.
- Unless otherwise stated assume the following:
 - * The oscillator frequency is precisely 2 MHz.
 - * The code should run on an **ATxmega128A1U** as configured on the Out of the Box uPAD and uPAD Base Board **without** any additional peripherals.
 - * You can assume the standard bit equates that I have used in class examples (e.g., BIT0 = 0b0000 0001, BIT76 = 0b1100 0000b, INV76 = 0b0011 1111) have already been done for you.



UF's NaviGator champion in Hawaii.



*May the Schwartz
be with you!*

Good luck and Go Gators!

PLEDGE:

On my honor as a University of Florida student, I certify that I have neither given nor received any aid on this examination, nor I have seen anyone else do so.

PRINT YOUR NAME

SIGN YOUR NAME

DATE (22 Feb 17)

Regrade comments below. Give page # & problem # and reason for the petition.	Pages	Available	Points
	2-4	40	
	5	8	
	6	11	
	7	11	
	8-9	15	
	10-11	15	
	TOTAL	100	

Exam 1

_____, _____
Last Name, First Name

- [40%] 1. Design a complete expansion to a XMEGA board (like your uPAD) by adding a **ROM**, an **SRAM**, an **input port**, an **output port**, and a **keypad**. Assume that each of the first four devices above can use **only** the address space from **0x03 2000** and **0x03 FFFF**. Complete the figure to the right and the table below for each of parts a-c.

2 min

(%)

6 min

- a) Add a **32K (32k x 8) ROM** in the given address range above. Use **only CS0** (this is the highest priority) if possible; if not, use as little additional logic gates (or PLDs) as necessary. As a second priority, place the ROM at the **lowest possible** addresses. Configure CS0 by specifying the below values. Add to the figure to the right and the table below.

EBI_CTRL =
CS0_CTRLA =
CS0_BASEADDRH =
CS0_BASEADDRL =

Port/Memory Blocks

(%)

4 min

- b) Also add an **8K (8k x 8) SRAM** somewhere in the given address range above. Use **only CS1** (this is the highest priority) if possible; if not, use as little additional logic gates (or PLDs) as necessary. As a second priority, place the SRAM at the **lowest possible** addresses. Add to the above right figure and the table below. (It is **not** necessary to calculate the CS1 control register values.)

(%)

4 min

- c) Also add an **input port** (In7-0) and an **output port** (Out7-0, at the same addresses as the input port) somewhere in the given address range above, filling up **all** the possible available address space. Use **only CS2** (this is the highest priority) if possible; if not, use as little additional logic (or PLDs) as necessary. As a second priority, place the ports at the **lowest possible** addresses. Add to the above right figure and the table below. (It is **not** necessary to calculate the CS2 control register values.)

32K (32k x 8) ROM Addr Range:

0x_____ - 0x_____ = 0b_____ - 0b_____

8K (8k x 8) SRAM Addr Range

0x_____ - 0x_____ = 0b_____ - 0b_____

Port Addr Range:

0x_____ - 0x_____ = 0b_____ - 0b_____

[illegible]









Exam 1

_____,
Last Name

_____,
First Name

- (%) 1. h) Complete the circuit diagram below as specified in part a-e and g. **Please USE LABELS instead of wires! Please USE LABELS instead of wires!** Add additional components **only** if necessary (but only resistors and SSI gates, e.g., ANDs, NORs, NOTs, etc.).

12 min

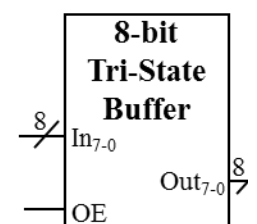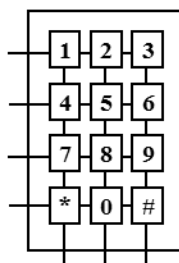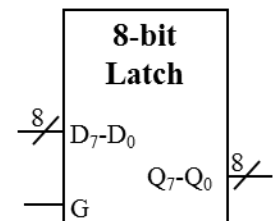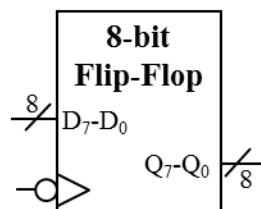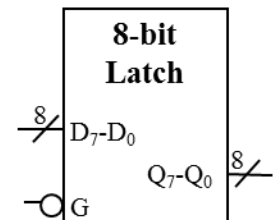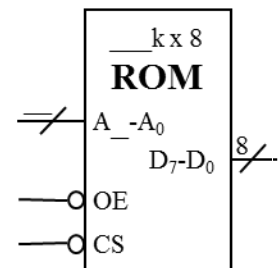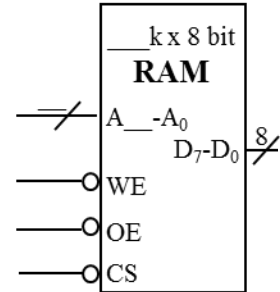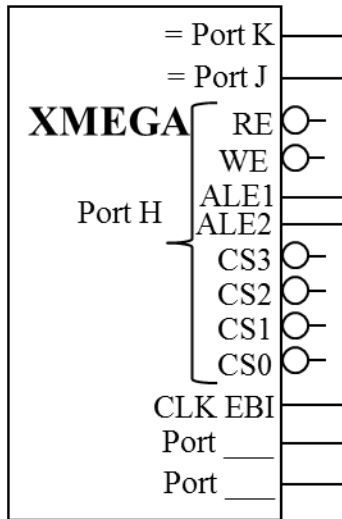


Exam 1

- [8%] 2. The **UF3744- μ C** is a new 8-bit microcontroller. The timing diagrams for reading and writing are shown here. Like many of the processors that we discussed in class, there is a time-multiplexed bus, in this case, for address and data. Note the two control signals on this device, E1 and E2.




10 min

Create a **complete circuit diagram** to add a 16K ($16k \times 8$) SRAM to the UF3744- μ C, starting at address 0x4000.

UF3744 Read Cycle

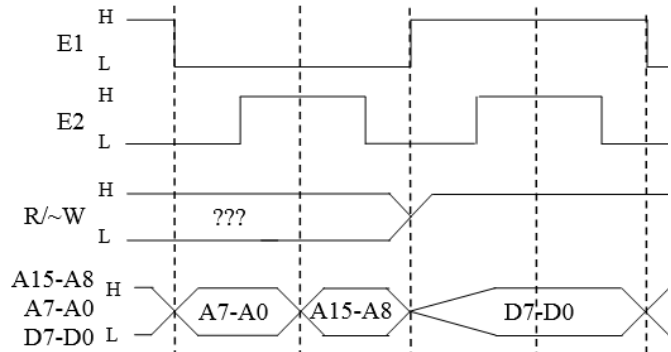

UF3744 Write Cycle

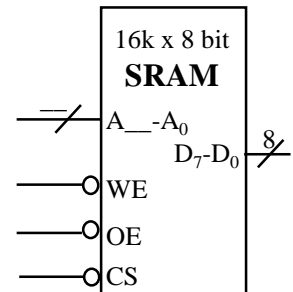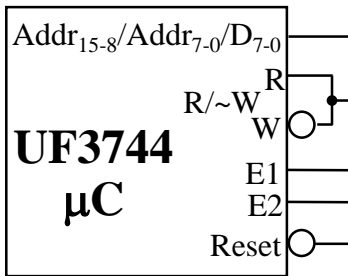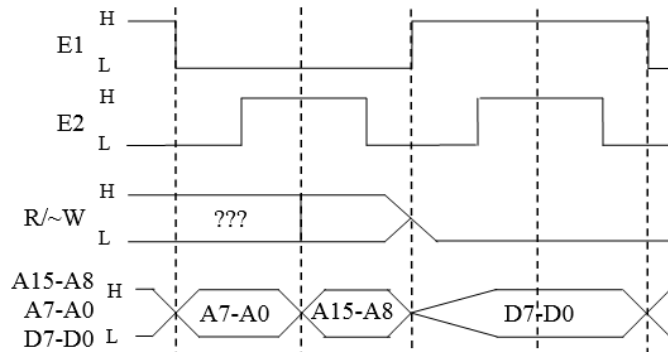

[illegible]

Exam 1

_____,
Last Name

_____,
First Name

[11%] 4. Answer or solve each of the following short questions.


(2%) a) Explain when and why the NOP was needed in the keypad lab.

2 min

(6%) b) Draw a complete **mixed-logic** circuit diagram to directly implement the below equation, i.e., do **NOT** simplify the equation. Include pin numbers on your diagram and use appropriate switch circuits and an LED circuit. Use switches, resistors and LED's as needed. The only IC (chip) you can use is the 74'27 (shown), but draw a **logic diagram** not a layout. Pick and label appropriate activation levels for A, B and Y. Show the switches in input's **true** positions. A block diagram of a 74'27 is shown to the right.

5 min

$$Y = /(A * /B)$$

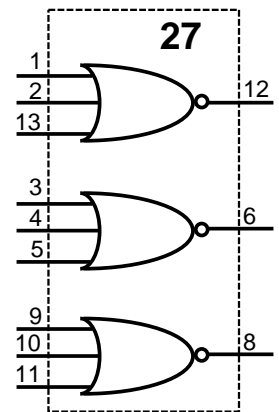

(3%) c) Explain how you might use an interrupt with the keypad and why this would be a better solution than what you did in lab. Note: You can also assume that an interrupting timer exists for whatever time you need.

4 min

[illegible]

[illegible]

